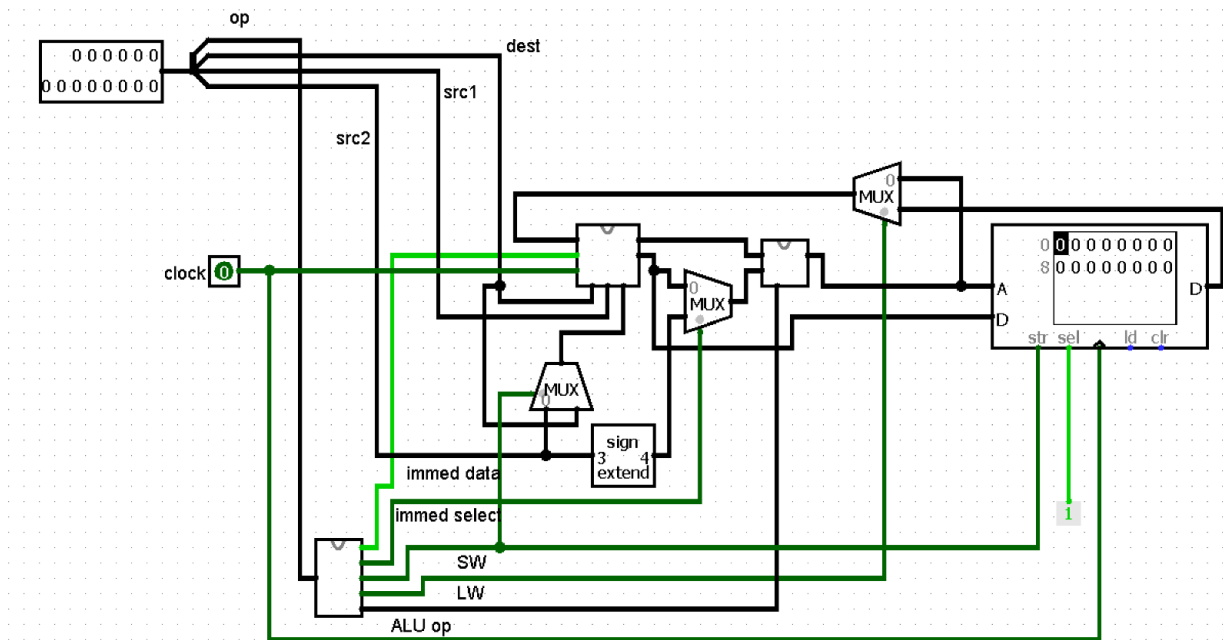


Testing the circuit (ALU with mem):





First instruction:

Poke a value like `d` into data memory location 0, then poke your instruction word so that it performs the equivalent of `lw $3 0($0)`. This should put the value `d` into register 3, presuming register 0 is 0 to begin with.

```
lw $3 0($0) = 1 0 1 00 011 000 000 (I/SW/LW/OP/WA/RA1/offset)
```



After rising clockedge:

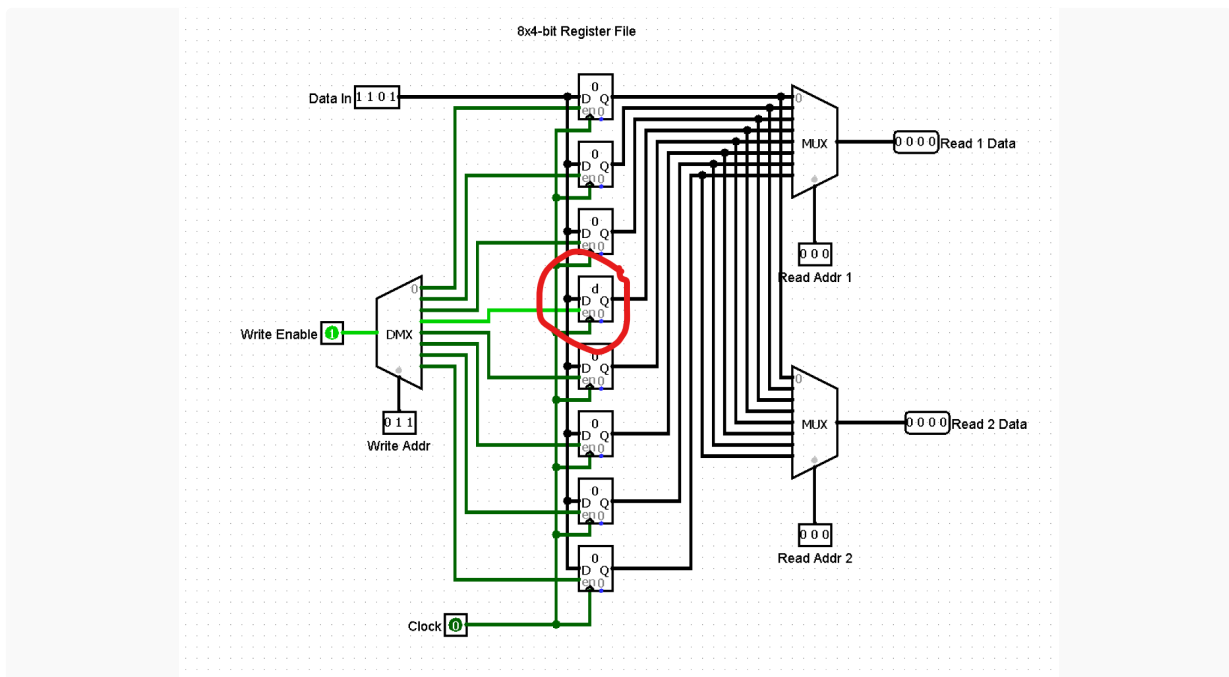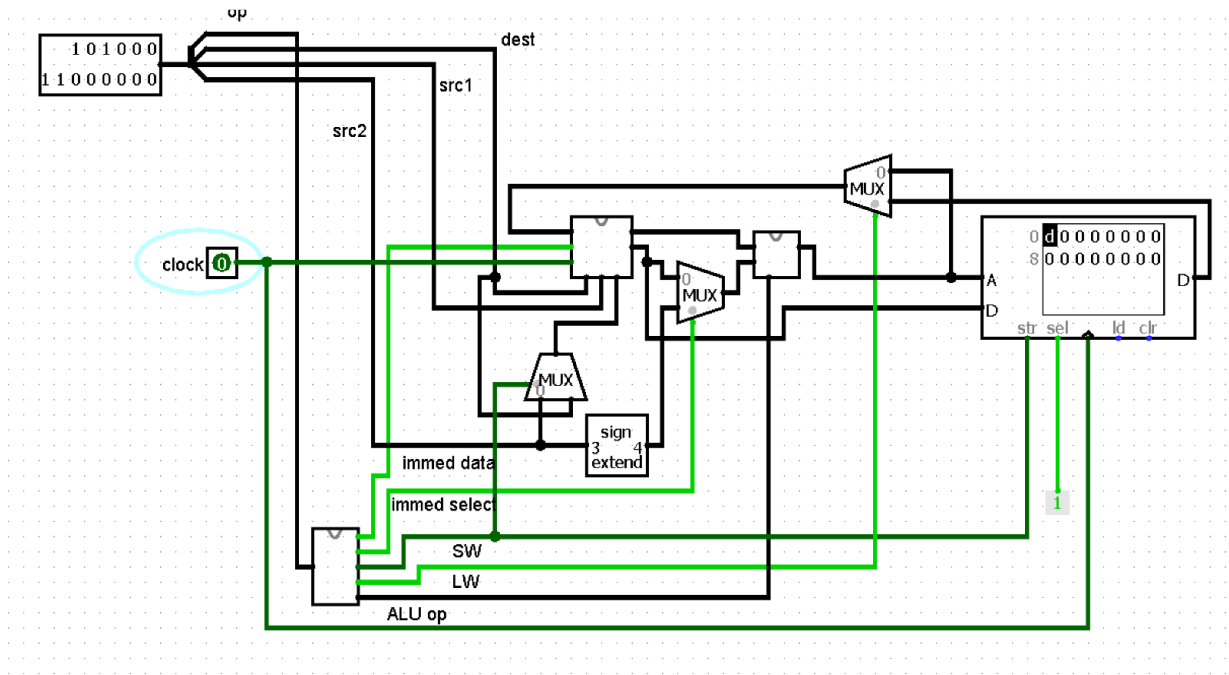

Second Address: Put a value like 'f' into register 2, then poke your instruction word bits so that it performs the equivalent of `sw $2 1($0)`. This should write the value `f` into memory address


`sw $2 1($0) = 1 1 0 00 010 000 001 (I/SW/LW/OP/RA2/RA1/offset)`

Before rising clock edge

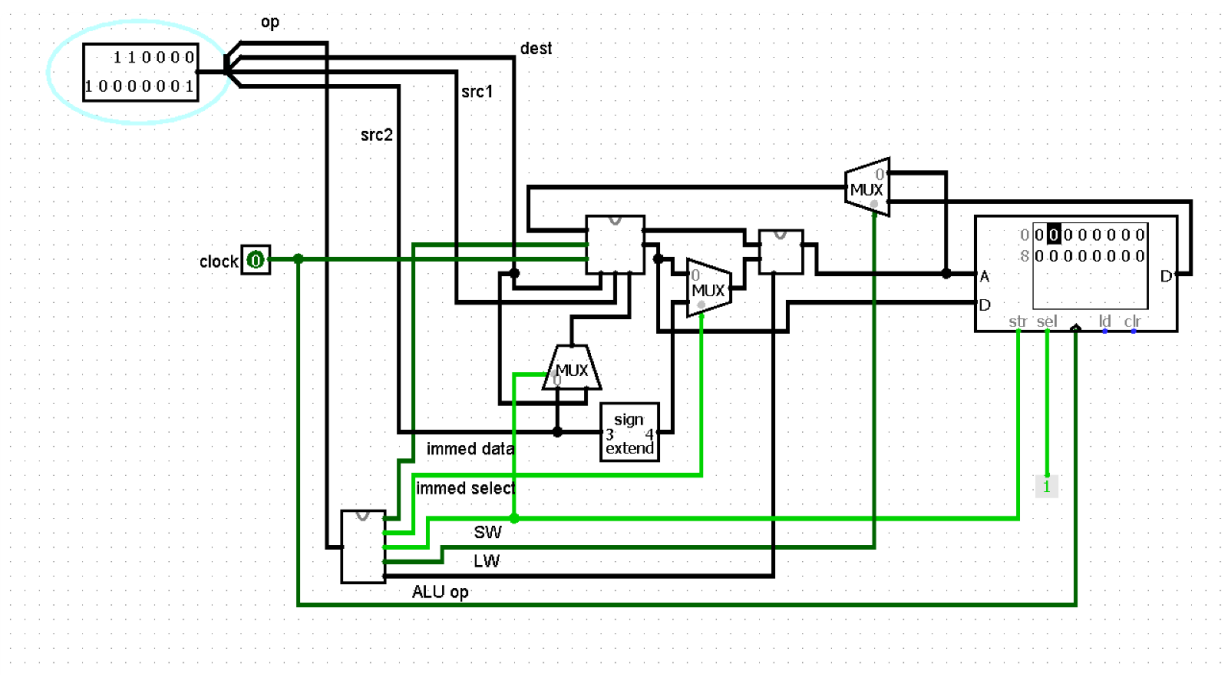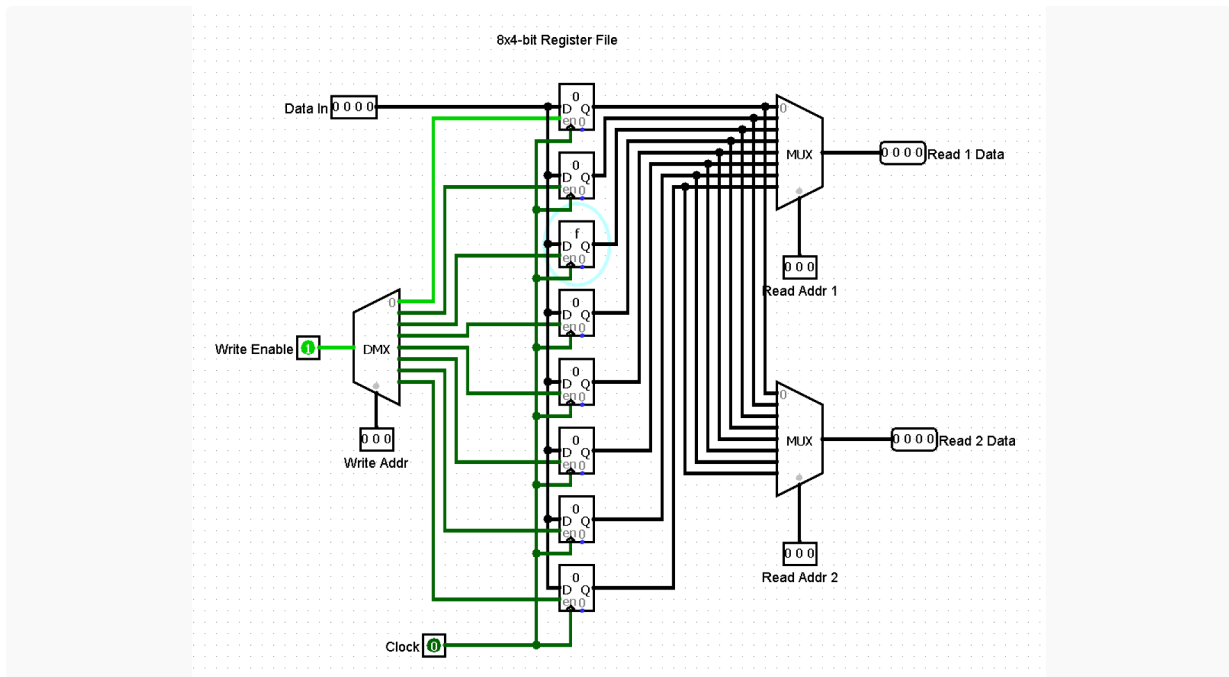

After rising clockedge:




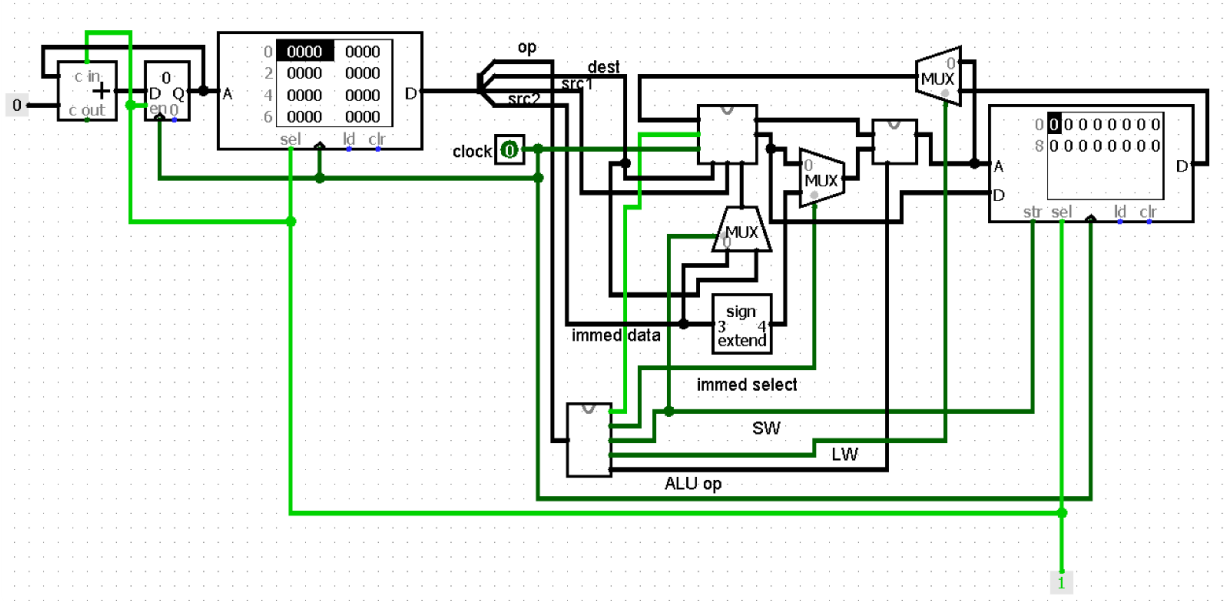


Testing;


1) Loading the 14-bit hex commands in the instruction memory


Before rising clock edge:

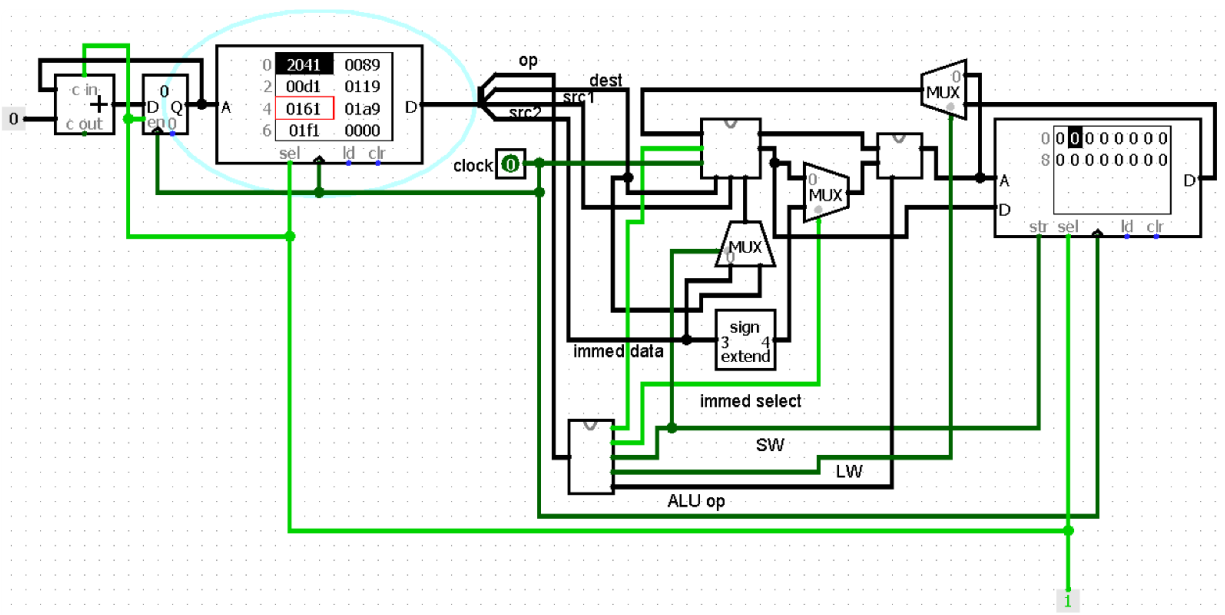

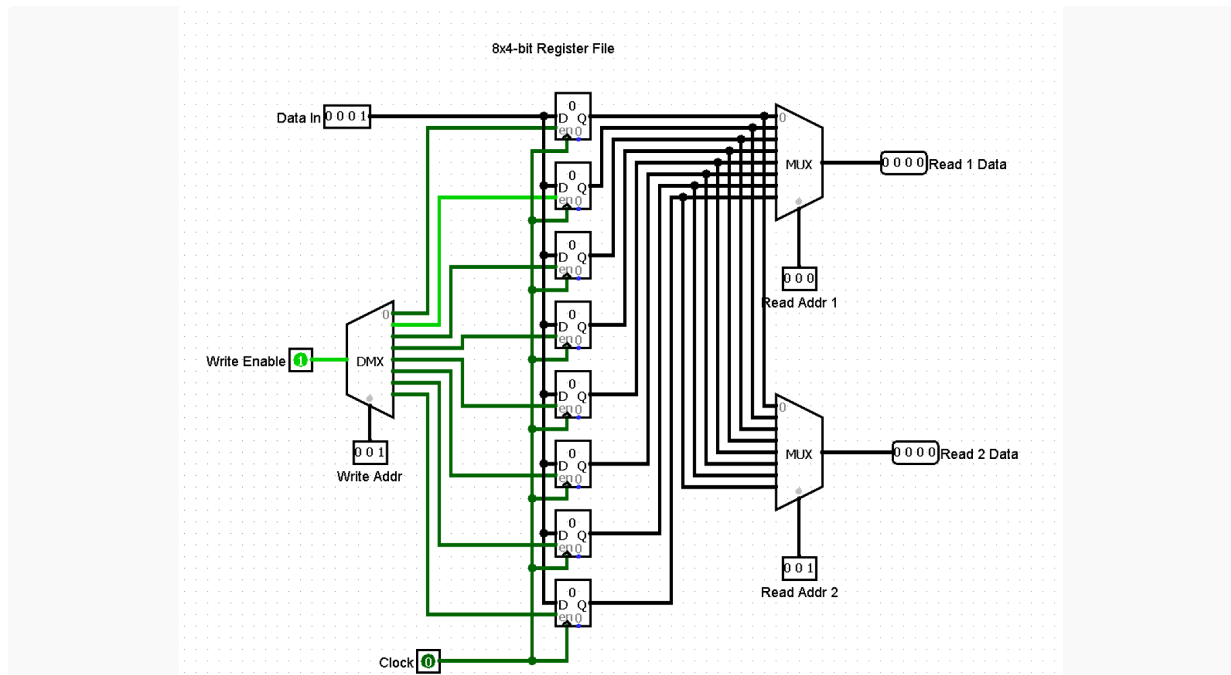

After multiple rising clockedges

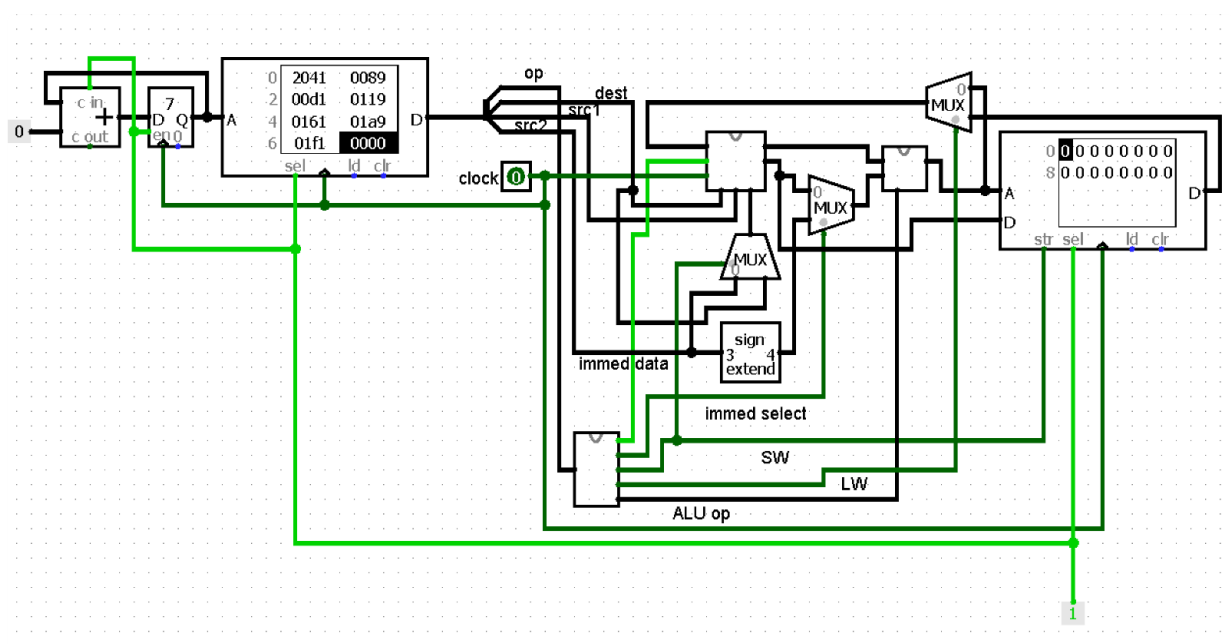

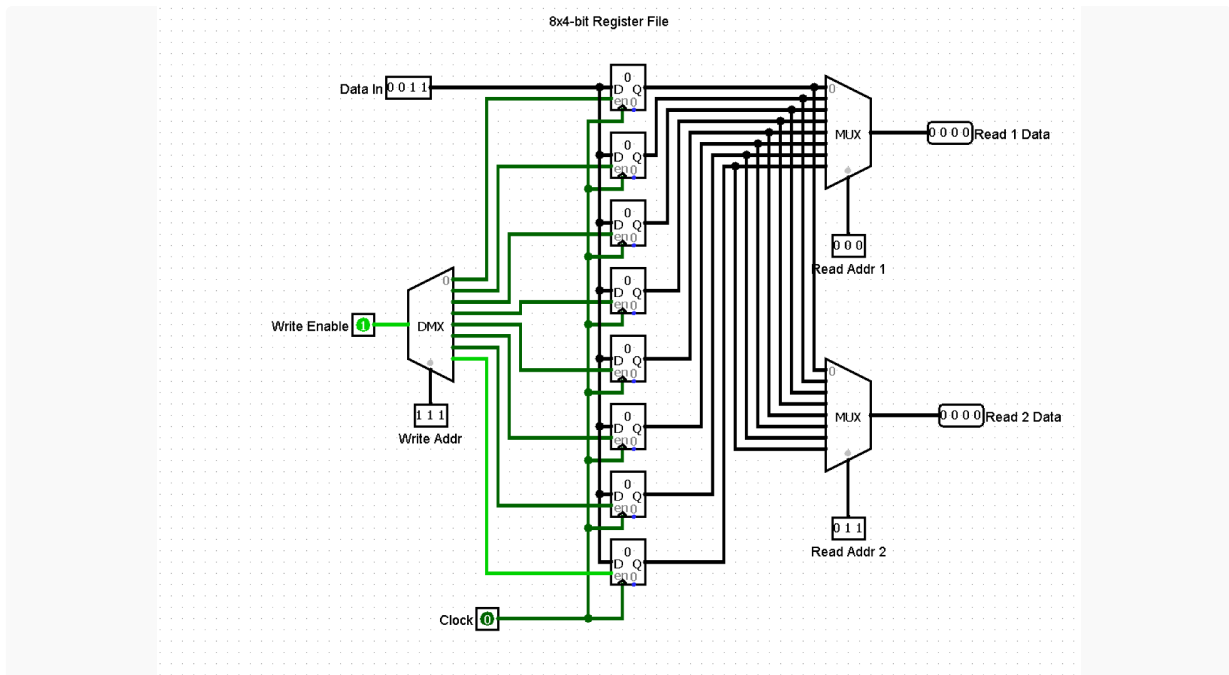

Running some cycles to finish all the load word instructions:

Now all alphabets a through f will be loaded in the registers:

